

2.4 Boolean Expressions and Gate Representations

Various coding languages use various symbols for NOT, AND, OR, and logical propositions.

Classical symbols

p, q, r

$\sim p$

$p \wedge q$

$p \vee q$

Boolean symbols

A, B, C

\bar{A}

AB (or $A \cdot B$)

$A+B$

Ex: Write as a Boolean expression:

$$p \wedge (q \vee \sim r)$$

$$A(B + \bar{C})$$

Order of Operations

NOT, then AND, then OR

Brackets override the order.

The negation bar also acts like brackets: do the operation under the bar then the negation.

Ex: What is the order of operations?

- a) $\bar{A}B+C$ NOT, AND, OR
- b) $A+\bar{BC}$ AND, NOT, OR
- c) $\overline{A+BC}$ OR, NOT, AND
- d) $(A+\bar{B})C$ NOT, OR, AND

Ex: Is $\overline{A+B}$ logically equivalent to $\bar{A}+\bar{B}$?

A	B	A+B	$\overline{A+B}$	\bar{A}	\bar{B}	$\bar{A}+\bar{B}$
0	0	0	1	1	1	1
0	1	1	0	1	0	1
1	0	1	0	0	1	1
1	1	1	0	0	0	0

Not identical

No. $\overline{A+B} \not\equiv \bar{A}+\bar{B}$

Ex: Simplify $AB + A\bar{B}$

A	B	AB	\bar{B}	$A\bar{B}$	$AB + A\bar{B}$
0	0	0	1	0	0
0	1	0	0	0	0
1	0	0	1	1	1
1	1	1	0	0	1


$$AB + A\bar{B} \iff A$$

Ex: Build the truth table for $A + \overline{B+C}$

A	B	C	$B+C$	$\overline{B+C}$	$A + \overline{B+C}$
0	0	0	0	1	1
0	0	1	1	0	0
0	1	0	1	0	0
0	1	1	1	0	0
1	0	0	0	1	1
1	0	1	1	0	0
1	1	0	1	0	0
1	1	1	1	0	0

A gate representation is a way to visualize logical expressions.

(AND)

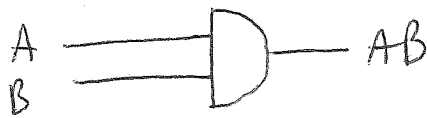


(OR)



(NOT)

An open circle is used for negation.

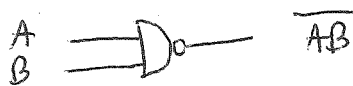


Ex: Draw the gate representation =


a) $A + \bar{B}$




b) $\overline{A + B}$

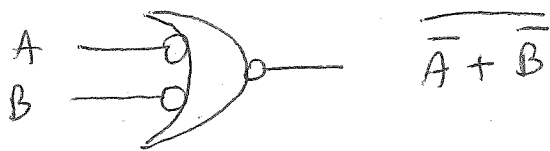

c) $\overline{A \bar{B}} + C$

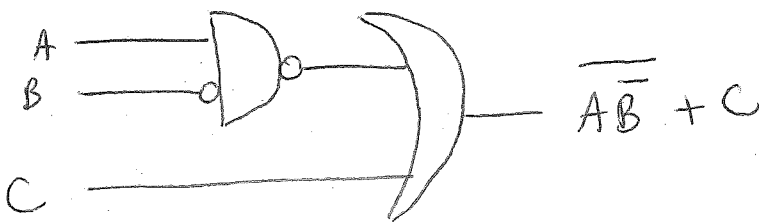

Also acceptable:

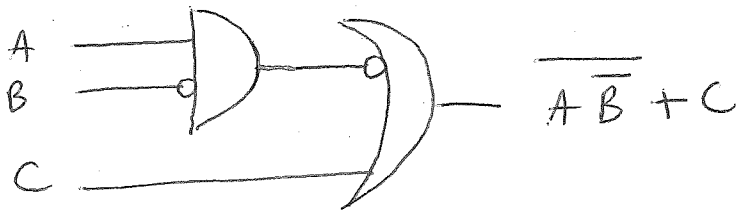

d) $A + \bar{B} \bar{C}$

